

**Group - E**

8. (a) An amplifier has voltage gain of 500 without feedback. Calculate the voltage gain with negative feedback, given that the feedback ratio is 0.04.
- (b) Write short notes on any three:
- Fermi Dirac distribution principle
  - Mass Action Law
  - Moore's Law
  - Barkhausen criterion
  - LED.
- 3 + (3 × 3) = 12**
9. (a) Explain the concept of virtual ground in an OPAMP. How is it different from a 'real' ground?
- (b) Draw the open loop characteristics of an OPAMP. Show how an OPAMP can be used as a voltage comparator.
- 5 + (2 + 5) = 12**

**BASIC ELECTRONICS  
(ECEN 1011)****Time Allotted : 3 hrs****Full Marks : 70*****Figures out of the right margin indicate full marks.******Candidates are required to answer Group A and any 5 (five) from Group B to E, taking at least one from each group.******Candidates are required to give answer in their own words as far as practicable.*****Group – A  
(Multiple Choice Type Questions)**

1. Choose the correct alternative for the following: **10 × 1 = 10**
- Zener breakdown occurs
    - mostly in Germanium junctions
    - due to rupture of covalent bonds
    - in lightly doped junctions
    - due to thermally generated minority carriers.
  - With increase of temperature in a p-n junction diode
    - Zener breakdown voltage increases while Avalanche breakdown voltage decreases
    - Both Zener breakdown voltage and Avalanche breakdown voltage decrease
    - Both Zener breakdown voltage and Avalanche breakdown voltage increase
    - Zener breakdown voltage decreases while Avalanche breakdown voltage increases.
  - The Q-point in a voltage amplifier is selected in the middle of the active region because
    - it gives better stability
    - the circuit needs a small dc voltage
    - the biasing circuit then needs less number of resistors
    - it gives distortion less output.
  - When the base width of a BJT becomes zero, the transistor is said to be in
 

(a) punch through	(b) cut off
(c) saturation	(d) breakdown.

- (v) In energy band diagram of n-type semiconductor, the donor energy level is  
 (a) slightly below conduction band (b) in conduction band  
 (c) slightly above valence band (d) in valence band.
- (vi) In a bridge rectifier, if  $V_m$  is the peak voltage across the secondary, the PIV is  
 (a)  $V_m$  (b)  $2V_m$   
 (c)  $V_m/2$  (d)  $V_m/\sqrt{2}$ .
- (vii) The CMRR of an ideal op amp is  
 (a) zero (b) infinity  
 (c) less than unity (d) greater than unity.
- (viii) The output of an integrator, for a step input is  
 (a) a ramp (b) a triangular waveform  
 (c) a spike (d) a pulse.
- (ix) Positive feedback is used in  
 (a) amplifiers (b) oscillators  
 (c) rectifiers (d) detectors.
- (x) The maximum rectification efficiency in case of full wave rectifier is  
 (a) 100% (b) 81.2%  
 (c) 66.6% (d) 40.6%.

**Group - B**

2. (a) Explain the operation of a centre tapped full wave rectifier with the help of a circuit diagram.  
 (b) The forward resistance  $R_F$  of a diode is  $20\Omega$ . This diode is used in a half wave rectifier circuit. The applied input voltage is  $v = 50\sin \omega t$  and load resistance  $R_L$  is  $800\Omega$ .  
 Determine:  
 (i) The dc load current  
 (ii) The dc power output  
 (iii) Rectification efficiency  
**6 + 6 = 12**
3. (a) Show how a Zener diode can be used as a reference diode in a circuit.  
 (b) A 12V, 0.36W Zener diode operates at a minimum current of 2mA. It is connected to a supply voltage of 15V with a series resistance R and a load resistance  $R_L$ . Calculate R and the range over which  $R_L$  can be varied.  
**7 + 5 = 12**

**Group - C**

4. (a) Why is the emitter region of a transistor more heavily doped than the base?  
 (b) Draw the common-base input characteristics of a transistor and explain the Early effect.  
 (c) An n-p-n transistor with  $\alpha$  of 0.98 is operated in the CB mode. Calculate the base current and the collector current if the emitter current is 3mA and the reverse saturation current is  $10\mu A$ .  
**2 + 6 + 4 = 12**
5. (a) What is transistor biasing? Mention the factors for determining the choice of the quiescent point.  
 (b) What is thermal runaway in BJTs? Justify the use of a self-bias circuit in improving the circuit stability.  
**(2 + 2) + (2 + 6) = 12**

**Group - D**

6. (a) Does any current flow through an n-channel enhancement and a depletion MOSFET with a zero gate-to-source voltage and a positive drain bias? Justify your answer. Draw the static characteristics of an n-channel MOSFET operated in both the enhancement and depletion modes.  
 (b) An n-channel enhancement mode MOSFET shows a saturation drain current of 5mA for  $V_{GS} = 8V$ . If the threshold voltage is 4V calculate the saturation drain current for  $V_{GS} = 10V$ .  
**(3 + 5) + 4 = 12**
7. (a) When is the channel of a JFET said to be pinched off. Explain pinch of voltage with the help of appropriate illustration.  
 (b) Draw the drain characteristics of a JFET, indicate the different regions of operation and explain how it can be used as a Voltage Variable Resistor (VVR).  
**6 + 6 = 12**